

招生學年度	103	招生類別	碩士班
系所班別	電機光電碩士班聯合招生（電機工程學系碩士班、電機工程學系電子工程碩士班、光電工程學系碩士班）		
科目名稱	電子學		
注意事項	本考科可使用掌上型計算機		

1. A Si pn junction employs  $N_A = 10^{16} \text{ cm}^{-3}$  and  $N_D = 2 \times 10^{15} \text{ cm}^{-3}$ . (a) Estimate the minority carrier concentrations on both sides at room temperature. (b) Sketch the electric field and potential in the pn junction with a reverse bias voltage  $V_R = 2 \text{ V}$ . (10%)
2. For the circuit shown in Fig. 1, assume the common-emitter current gain of the BJT is 100, and neglect the Early effect. Find  $R_{in}$  and  $v_o/v_{sig}$ . (12%)

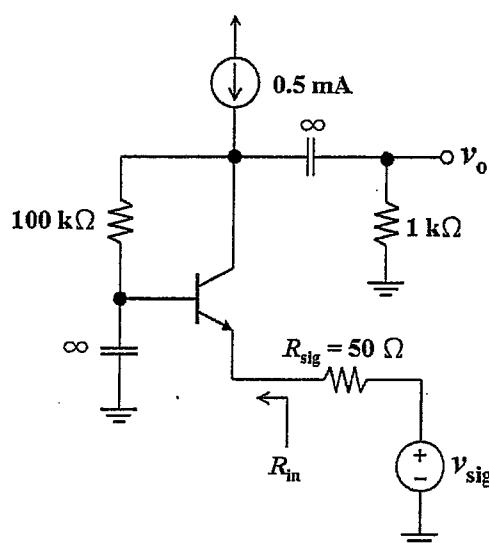


Fig. 1

3. Draw a cross section of a CMOS inverter. Clearly indicate source, drain, gate, oxide, n-type and p-type regions, and input and output terminals. (10%)
4. Fig. 2 shows a MOS amplifier with  $V_t = 0.5 \text{ V}$  and  $k_n'(W/L) = 2 \text{ mA/V}^2$ . Neglect the channel length modulation effect. (a) Find dc values of  $V_{GS}$ ,  $I_D$ , and  $V_D$ . (b) Find  $g_m$ ,  $R_{in}$ ,  $R_{out}$ , and  $v_o/v_{sig}$ . (18%)

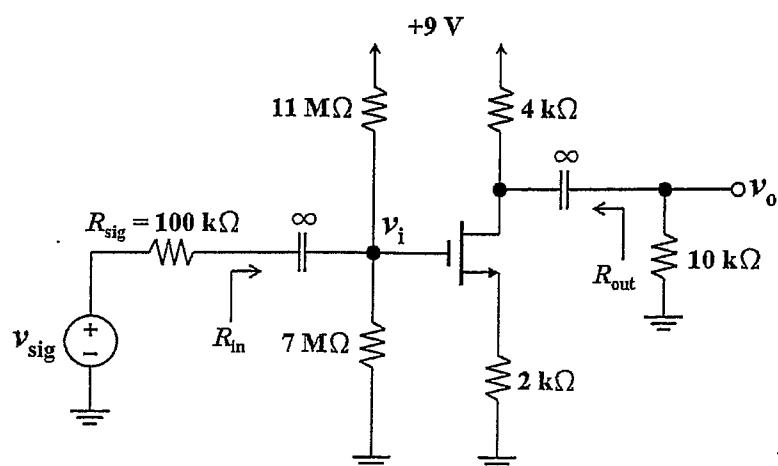


Fig. 2

招生學年度	103	招生類別	碩士班
系所班別	電機光電碩士班聯合招生（電機工程學系碩士班、電機工程學系電子工程碩士班、光電工程學系碩士班）		
科目名稱	電子學		
注意事項	本考科可使用掌上型計算機		

5. The PMOS cascode of Fig. 3 is designed for a given output impedance  $R_{out}$ . Explain what happens to  $R_{out}$  if the widths of all transistors are increased by a factor of N while the transistor lengths and bias currents remain unchanged. Assume channel-length modulation parameter  $\lambda$  is inversely proportional to channel length. Also assume all transistors operate in saturation and  $g_m r_o \gg 1$ . (15%)

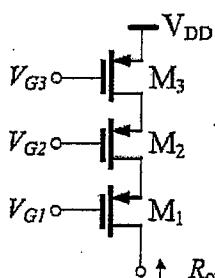


Fig. 3

6. (a) If a resistance has appeared in series with the source of MOSFET as shown in Fig. 4(a), determine the input and output poles of the circuit. Assuming  $\lambda = 0$ , and neglecting other capacitances except for  $C_{in}$  and  $C_L$ . (b) Repeat (a) for the circuit shown in Fig. 4(b). (20%)

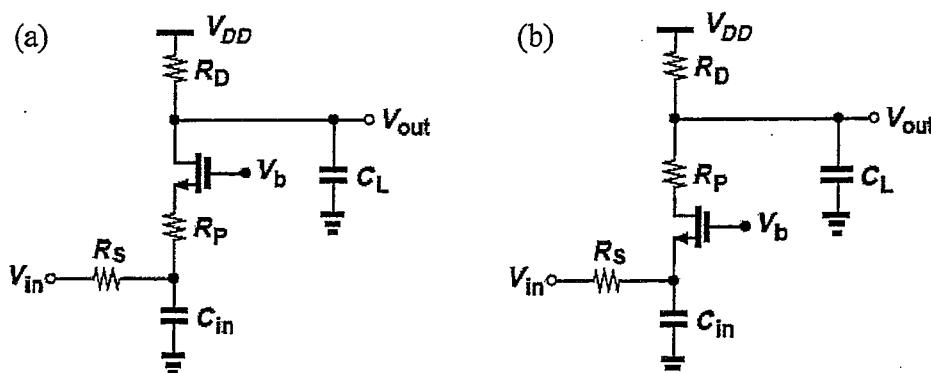


Fig. 4

7. Compute the input impedance  $R_{in}$  and output impedance  $R_{out}$  of the circuit shown in Fig. 5. Assume  $R_1 + R_2 \gg R_D$ . (15%)

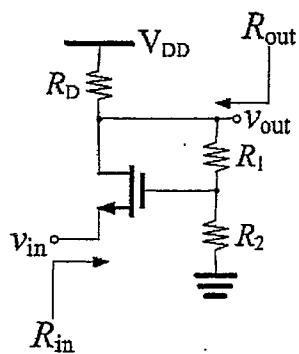


Fig. 5